

Elektronik Devreler I

Doç. Dr. Revna ACAR
VURAL

1.Ödev

Alırıza BİLİR

No:18014125

17 NİSAN 2022




S1)

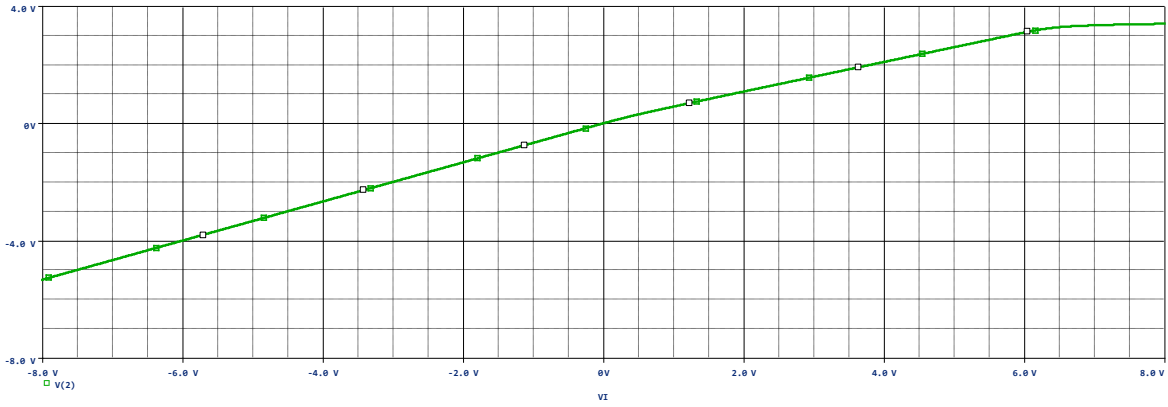
A) Simülasyon Kodu

```
ED1-1.cir (active) × ED1-1.dat (active) ×  
*Alınza Bilir  
VI 1 0 DC 0  
VE 4 0 DC 3V  
  
R1 1 2 20k  
R2 2 0 40k  
R3 3 0 40k  
  
D1 2 3 D1N4001  
D2 2 4 D1N4001  
  
.model D1N4001 D (IS=29.5E-9 RS=73.5E-3 N=1.96 CJO=34.6P VJ=0.627 M=0.461 BV=60 IBV=10U)  
.DC VI -8 8 0.001  
.probe  
.END
```


$V_O = f(V_I)$ gerilim transfer karakteristiği simülasyon sonucu:



B)

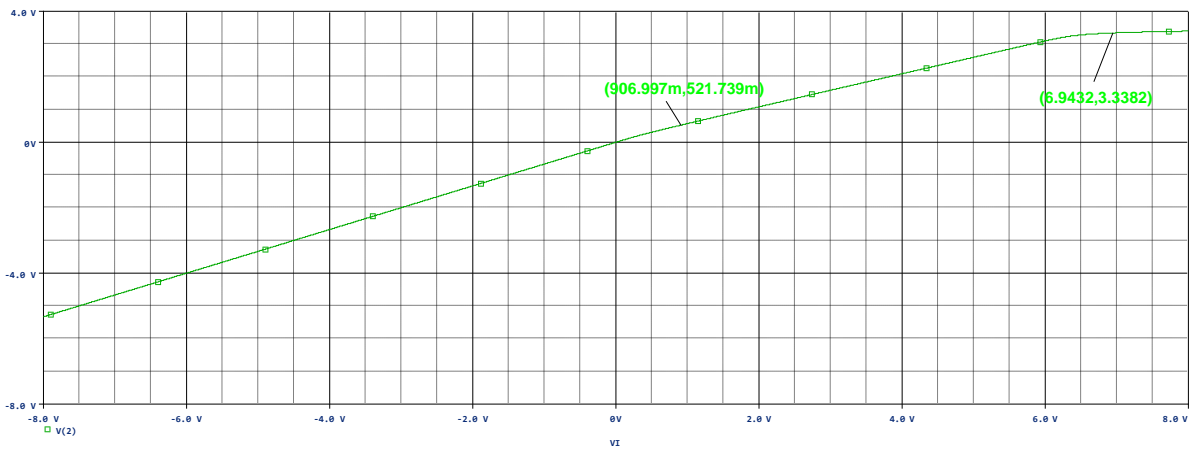


$V_0 < 0,627$ iken D_1 : OFF D_2 : OFF

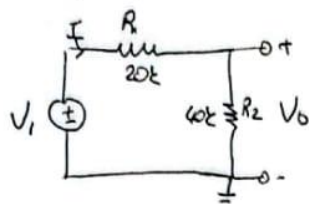

$$\left. \begin{aligned} V_0 &= I \cdot R_2 = I \cdot 40k \\ I &= \frac{V_1}{R_1 + R_2} = \frac{V_1}{60k} \end{aligned} \right\} V_0 = \frac{2}{3} V_1 \quad (1)$$

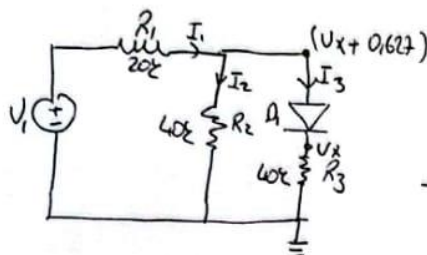$3,627 > V_0 \geq 0,627$ iken D_1 : ON D_2 : OFF



$$\begin{aligned} I_1 &= I_2 + I_3 \\ \frac{V_1 - 0,627 - V_x}{R_1} &= \frac{V_x + 0,627}{R_2} + \frac{V_x}{R_3 + R_{on}} \end{aligned}$$

$$\Rightarrow \frac{V_1 - 0,627 - V_x}{20k} = \frac{V_x + 0,627}{40k} + \frac{V_x}{40k + 735 \times 10^{-3}}$$

$$\Rightarrow V_1 = 2V_x + 0,9405 \Rightarrow V_x = \frac{V_1 - 0,9405}{2} = \frac{V_1}{2} - 0,47025$$

$$V_0 = V_x + 0,627 = \frac{V_1}{2} + 0,15675 \quad (2)$$

$V_0 = 0,627$ iken:

$$(2) \quad 0,627 = \frac{V_1}{2} + 0,15675$$

$$V_1 = 0,9405$$


$$(1) \quad 0,627 = \frac{2}{3} V_1$$

$$V_1 = 0,9405$$

$V_1 = -8$ iken:

$$(1) \quad V_0 = \frac{2}{3} (-8) \approx -5,33$$
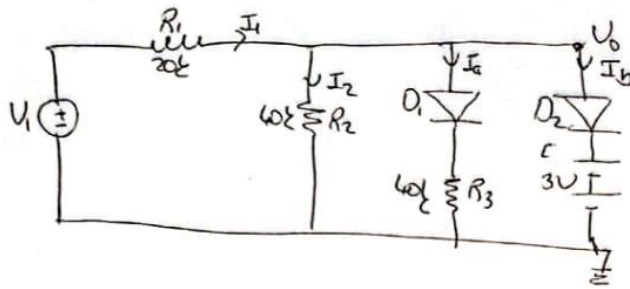
$$V_0 \geq 3,627 \text{ iken } D_1: ON \quad D_2: ON$$



$$I_1 = I_2 + I_q + I_b$$

$$\frac{V_1 - V_0}{R_1} = \frac{V_0}{R_2} + \frac{V_0 - 0,627}{R_3 + R_{s1}} + \frac{V_0 - 3,627}{R_{s2}}$$

$$\Rightarrow \frac{V_1 - V_0}{20k} = \frac{V_0}{40k} + \frac{V_0 - 0,627}{40k + 73,5 \times 10^{-3}} + \frac{V_0 - 3,627}{73,5 \times 10^{-3}} \quad (3)$$

$$V_0 = 3,627 \text{ iken}$$

$$(3) \quad V_1 = 6,9405$$

$$(2) \quad 3,627 = \frac{V_1 + 0,15675}{2}$$

$$V_1 = 6,9405$$

$$V_1 = 8 \text{ iken}$$

$$(3) \quad V_0 = 3,627$$

$$-8 < V_1 < 0,9405$$

D_1 : off

$$V_1 = -8 \Rightarrow V_0 = -5,33$$

D_2 : off

$$V_1 = 0,9405 \Rightarrow V_0 = 0,627$$

$$0,9405 \leq V_1 < 6,9405$$

D_1 : ON

$$V_1 = 6,9405 \Rightarrow V_0 = 3,627$$


D_2 : off

$$V_1 = 8 \Rightarrow V_0 = 3,627$$

$$6,9405 \leq V_1 < 8$$

D_1 : ON

D_2 : ON

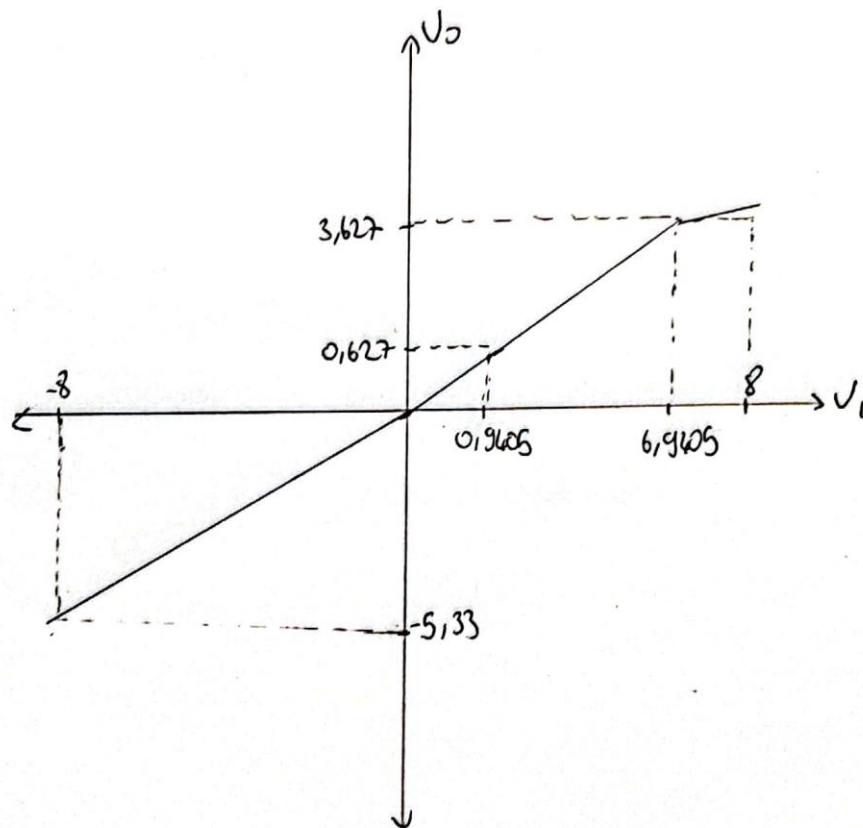

c)

IS	Saturation current (tıkama akımı)
RS	Series resistance
N	Emission coefficient
TT	Transit time
CJO	Zero-bias junction capacitance (tdD'deki jonksiyon kapasitesi)
VJ	Junction potential
M	Junction grading coefficient
EG	Activation energy:
XTI	IS temperature exponent
KF	Flicker noise coefficient
AF	Flicker noise exponent
FC	Forward bias depletion capacitance coefficient
BV	Reverse breakdown voltage
IBV	Reverse breakdown current

52 |

$$V_1 = \frac{25}{25} + 1 = 2$$

$$V_2 = 8,5 - \frac{25}{25} = 7,5$$

$$-V_2 < V_I < V_1 \text{ erfüllt, } V_I = V_0 *$$

$$V_I \geq V_1 = 2 \text{ ist:}$$

$$V_0 - 6 = \left(\frac{6 - V_1}{10 - V_1} \right) (V_I - 10)$$

$$V_0 - 6 = \left(\frac{6 - 2}{10 - 2} \right) (V_I - 10)$$

\downarrow
0,5

$$V_I \geq V_1 = 2, \quad V_0 = 0,5 V_I + 1 *$$

$$V_I \leq -V_2 = -7,5 \text{ ist:}$$


$$V_0 + 9 = \left(\frac{-9 + V_2}{-10 + V_2} \right) (V_I + 10)$$

$$V_0 + 9 = \left(\frac{-9 + 7,5}{-10 + 7,5} \right) (V_I + 10)$$

\downarrow
0,6

$$V_I \leq V_2, \quad V_0 = 0,6 V_I - 3 *$$

$$V_I \geq V_1 = 2 \text{ V}$$

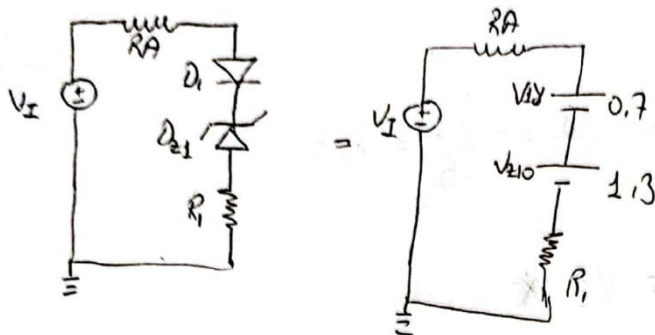


$$\frac{10}{R_A + R_1} < 5 \text{ mA}$$

$$R_A + R_1 > 2 \text{ k}\Omega$$

$$\frac{R_1}{R_A + R_1} = 0.5 \text{ (estim.)}$$

$$V_I \leq V_2 = -7.5 \text{ V}$$

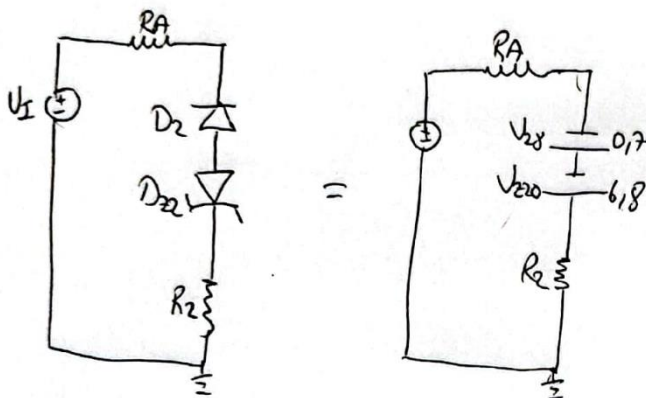


$$\frac{10}{R_A + R_2} < 5 \text{ mA}$$

$$R_A + R_2 > 2 \text{ k}\Omega$$

$$\frac{R_2}{R_A + R_1} = 0.6 \text{ (estim.)}$$
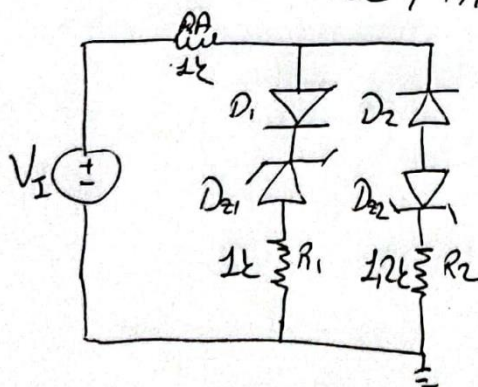
$$R_A = 1 \text{ k}\Omega, R_2 = 1.2 \text{ k}\Omega, R_1 = 1 \text{ k}\Omega$$



$$D_1 (V_D = 0.7 \text{ V}, r_D = 0)$$

$$D_2 (V_D = 0.7 \text{ V}, r_D = 0)$$

$$D_{z1} (V_{Dz1} = 1.3 \text{ V}, r_{Dz1} = 0)$$

$$D_{z2} (V_{Dz2} = 6.8 \text{ V}, r_{Dz2} = 0)$$